


$$V = IR \quad I = GU$$


$$\sigma = \frac{ne^2\tau}{m^*}$$

$$\vec{j} = \sigma \vec{E}$$


$$\rho = \frac{1}{\sigma} \approx T$$

$$P = RI^2$$

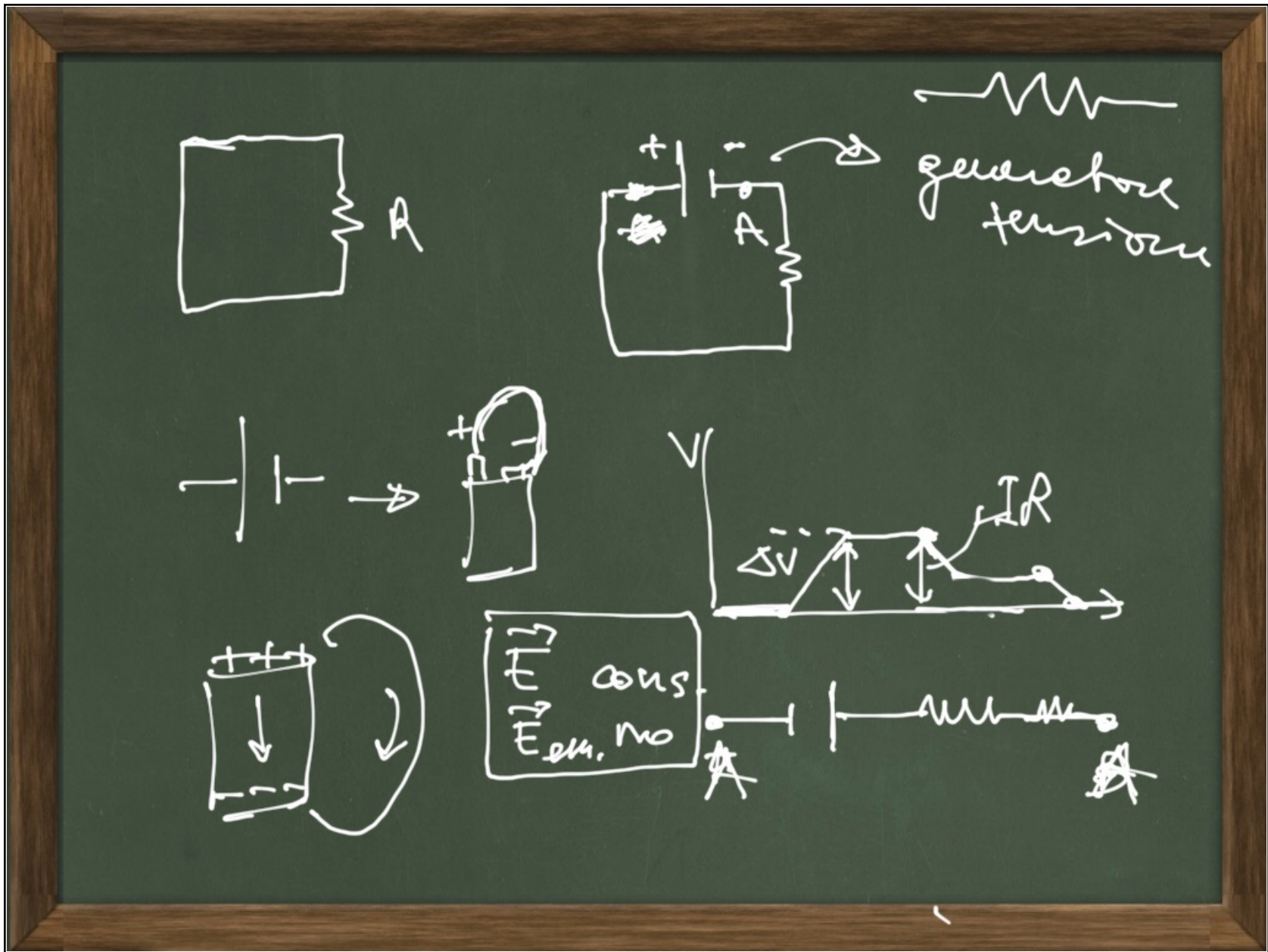

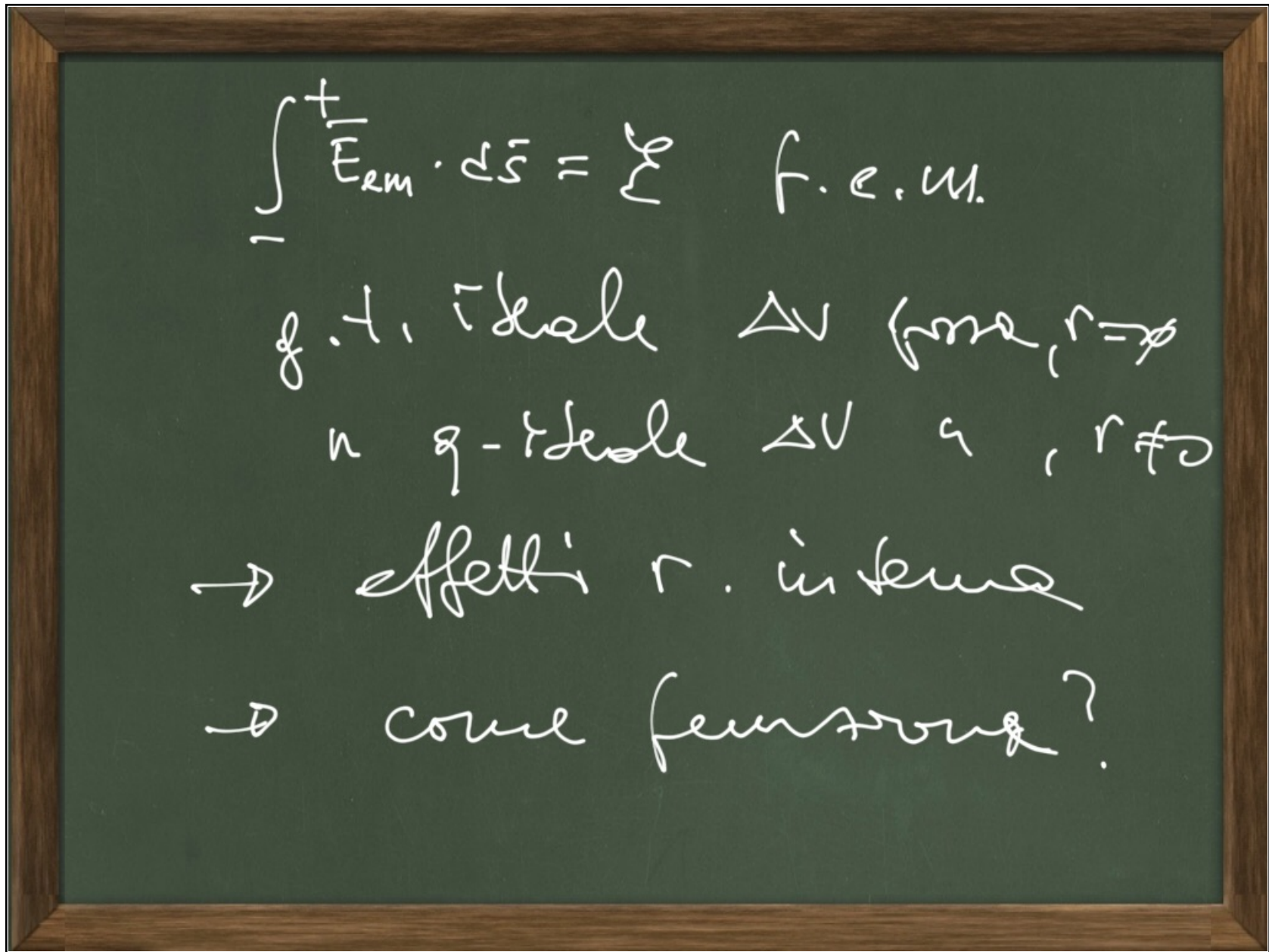

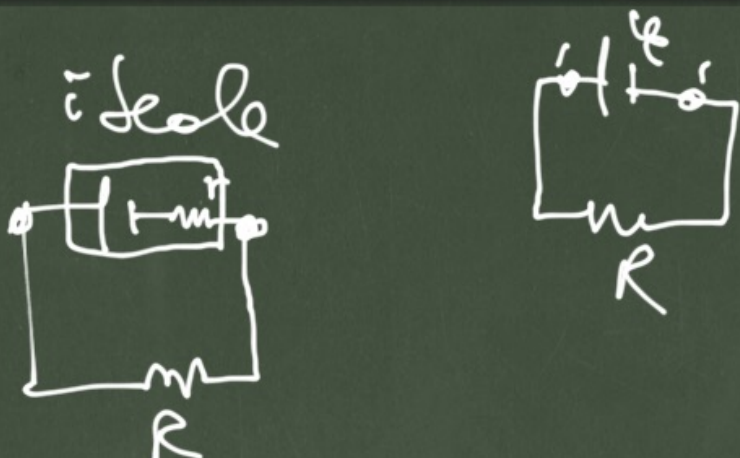$V = \mathcal{E} = RI$ ideal
 \mathcal{E} - ideal \rightarrow




$\mathcal{E} = (r + R)I$
 $P = (r + R)I^2 = \frac{\mathcal{E}^2}{(r + R)}$; $\eta = \frac{P_o}{P} = \frac{R}{R + r}$
 $P_c = RI^2 = \frac{R}{(R + r)^2} \mathcal{E}^2$; $\eta = \frac{1}{1 + \frac{r}{R}}$


$$\frac{C_0^2 R}{(r+R)^2} \rightarrow \frac{dP}{dR} = C_0^2 \frac{(r+R)^2 - 2(r+R)R}{(r+R)^4}$$


$$\frac{r^2 + 2rR + R^2 - 2rR - 2R^2}{(r+R)^4}$$


$$\frac{r^2 - R^2}{(r+R)^4} = \frac{(r+R)(r-R)}{(r+R)^4} = \frac{r-R}{(r+R)^3}$$


$$\text{max } P \Rightarrow r=R$$

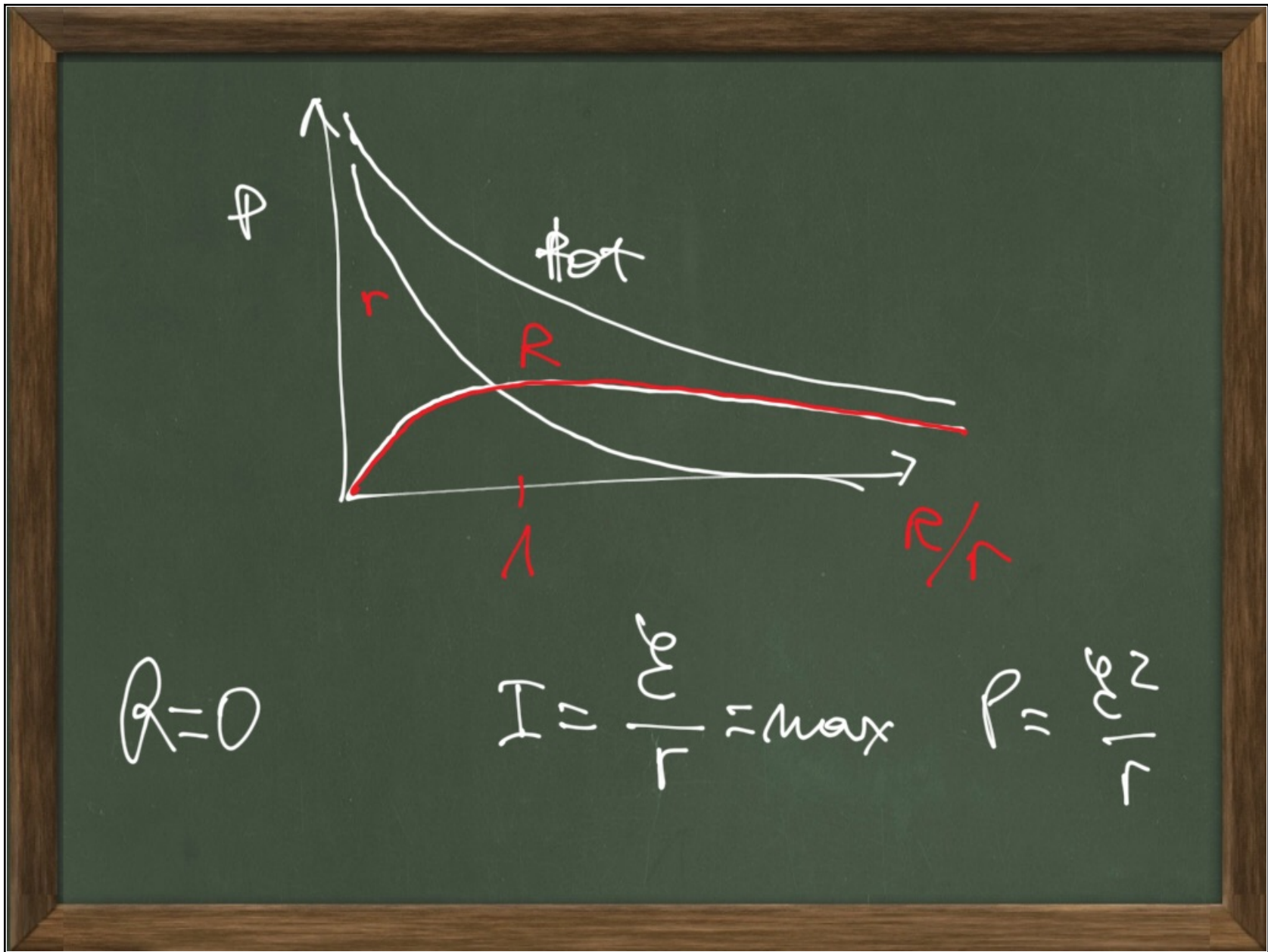

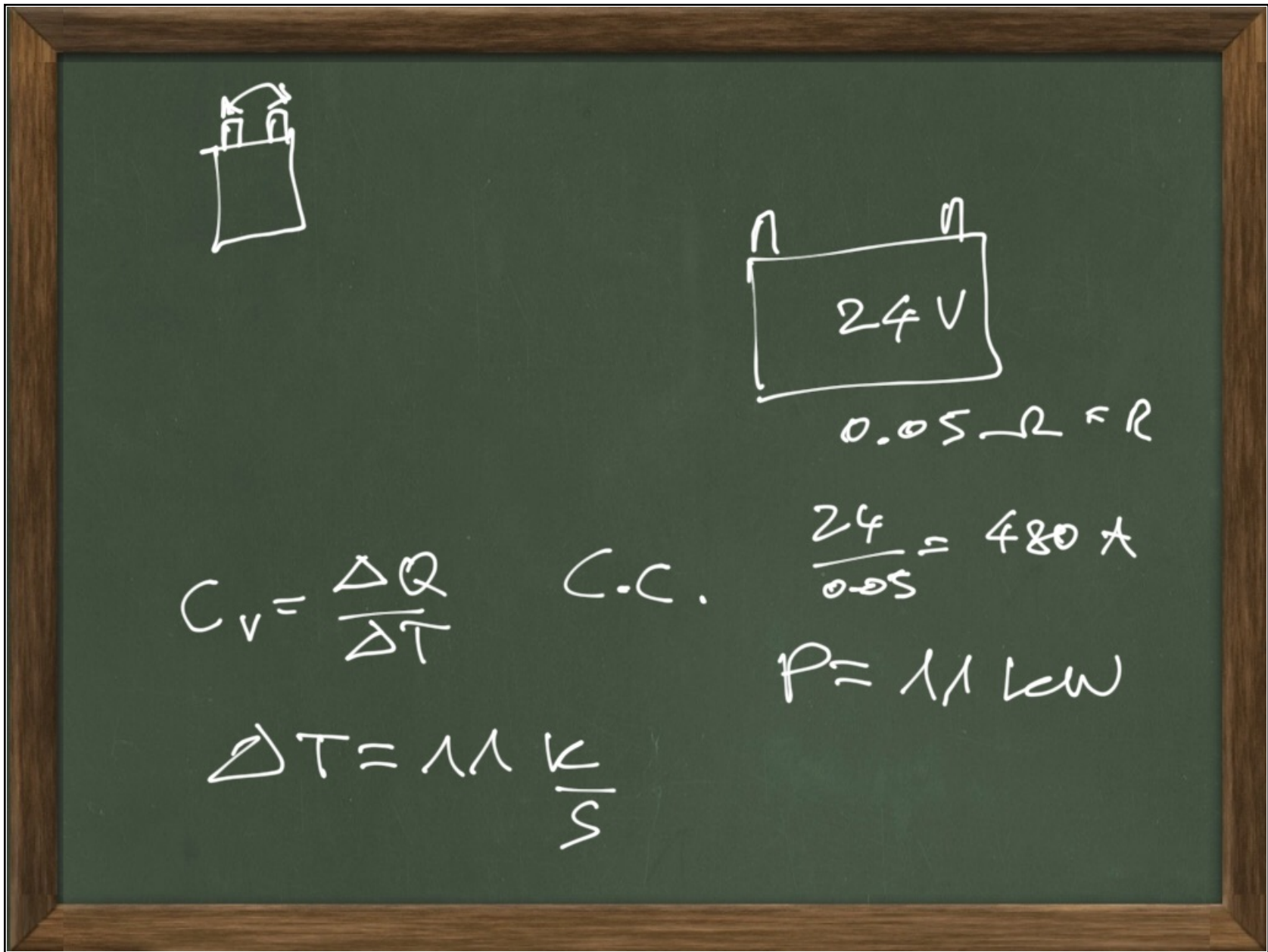

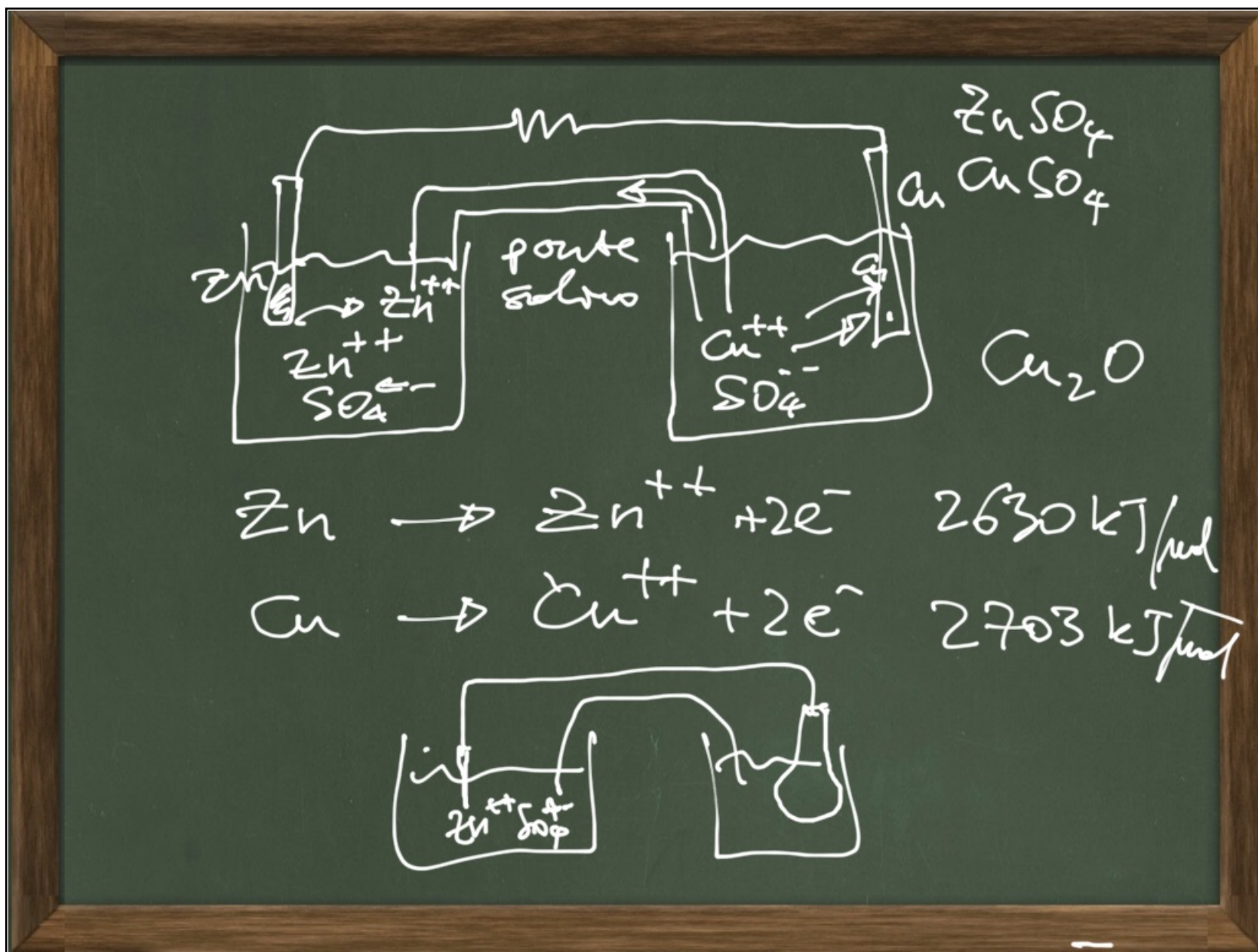

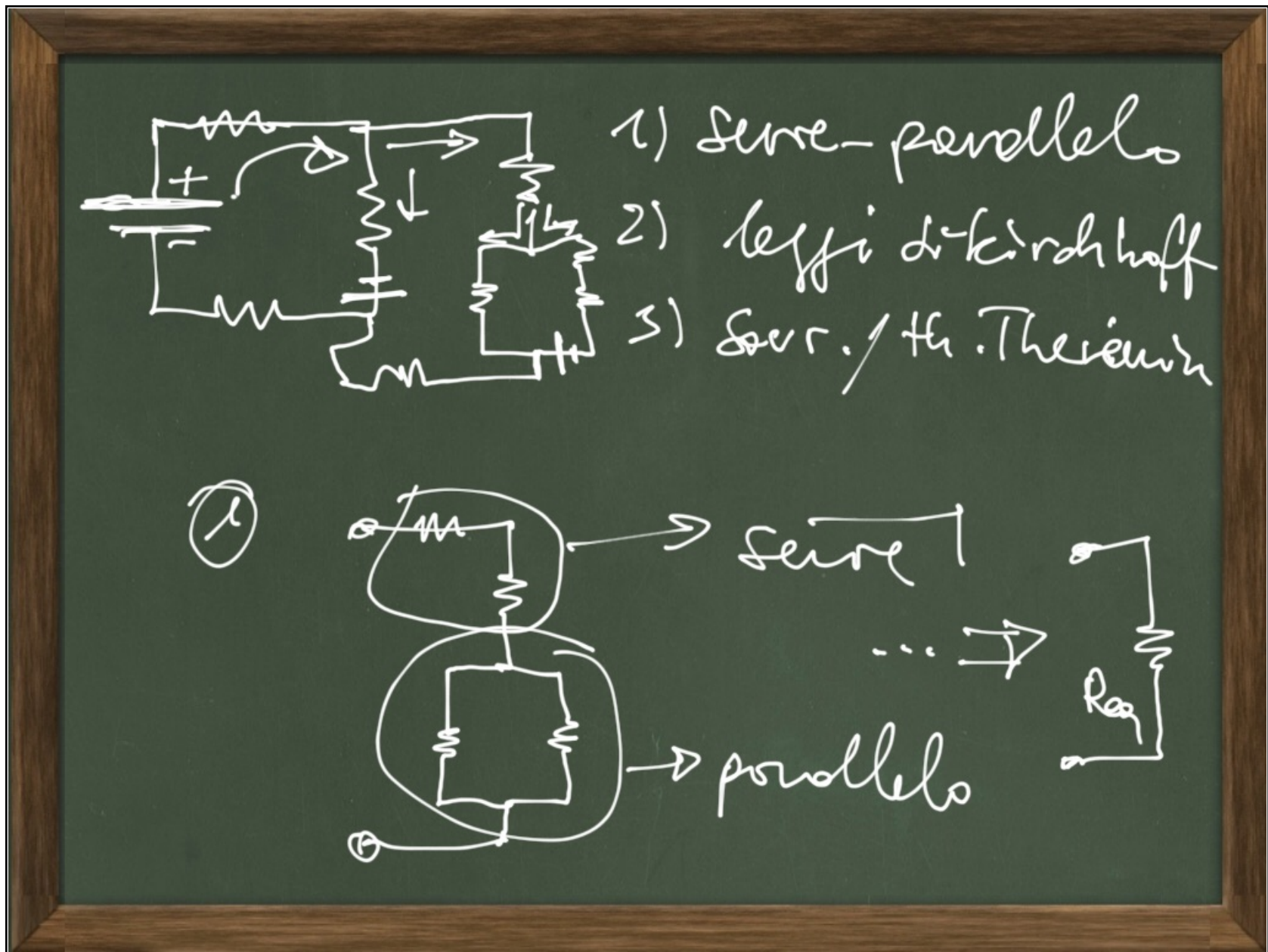

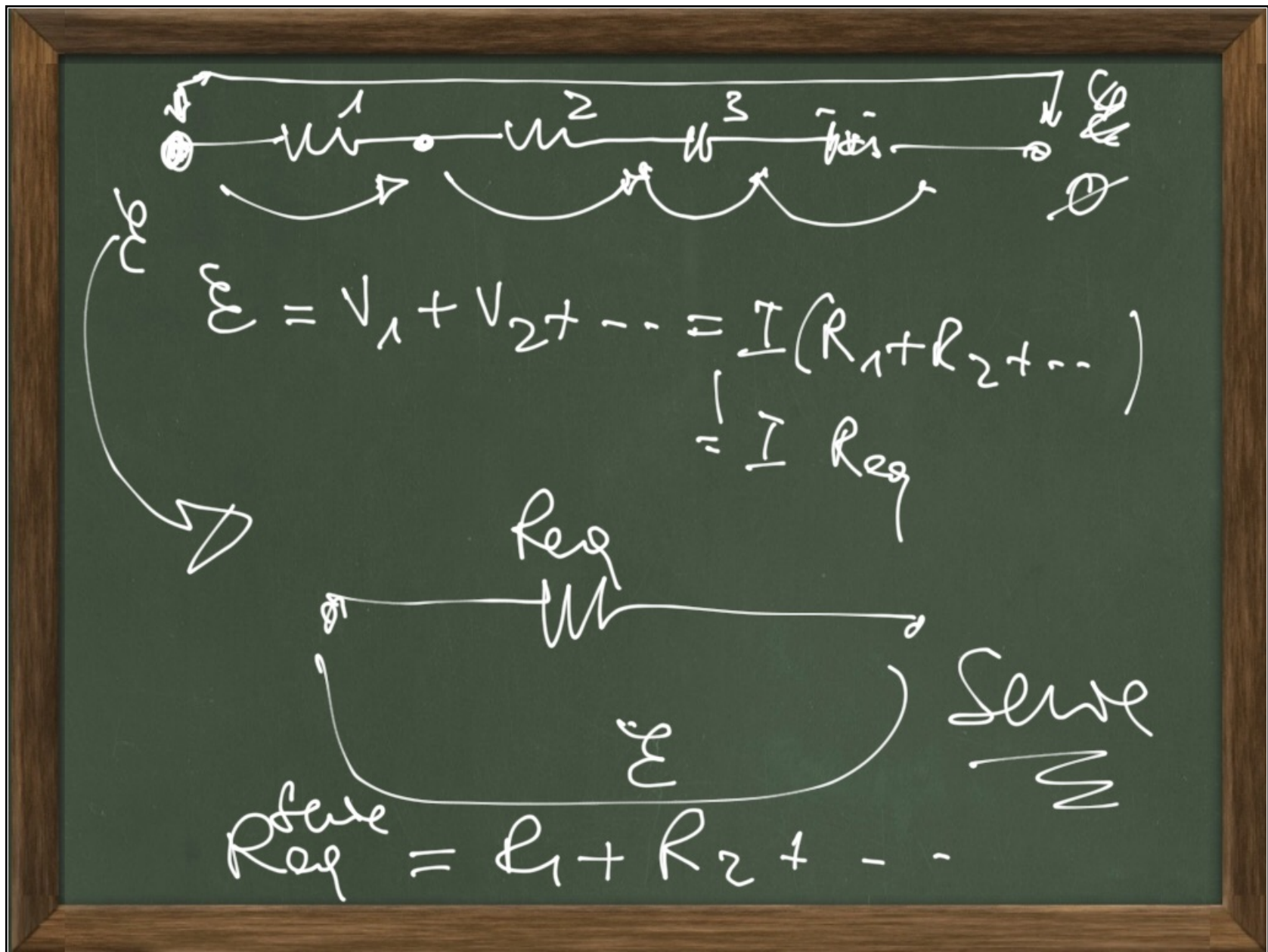

The image shows a chalkboard with handwritten notes on parallel circuits. On the left, a circuit diagram shows three resistors, labeled R_1 , R_2 , and R_3 , connected in parallel. A current I enters from the left, and the circuit is connected to terminals ϕ at the top and bottom. To the right of the diagram, the following equations are written:


$$V = R_1 I_1 = R_2 I_2 = \dots$$


$$I = I_1 + I_2 + \dots$$


$$I = \frac{V}{R_1} + \frac{V}{R_2} + \dots = \frac{V}{R_{eq}^{par}}$$


$$\frac{1}{R_{eq}^{par}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$


PAR

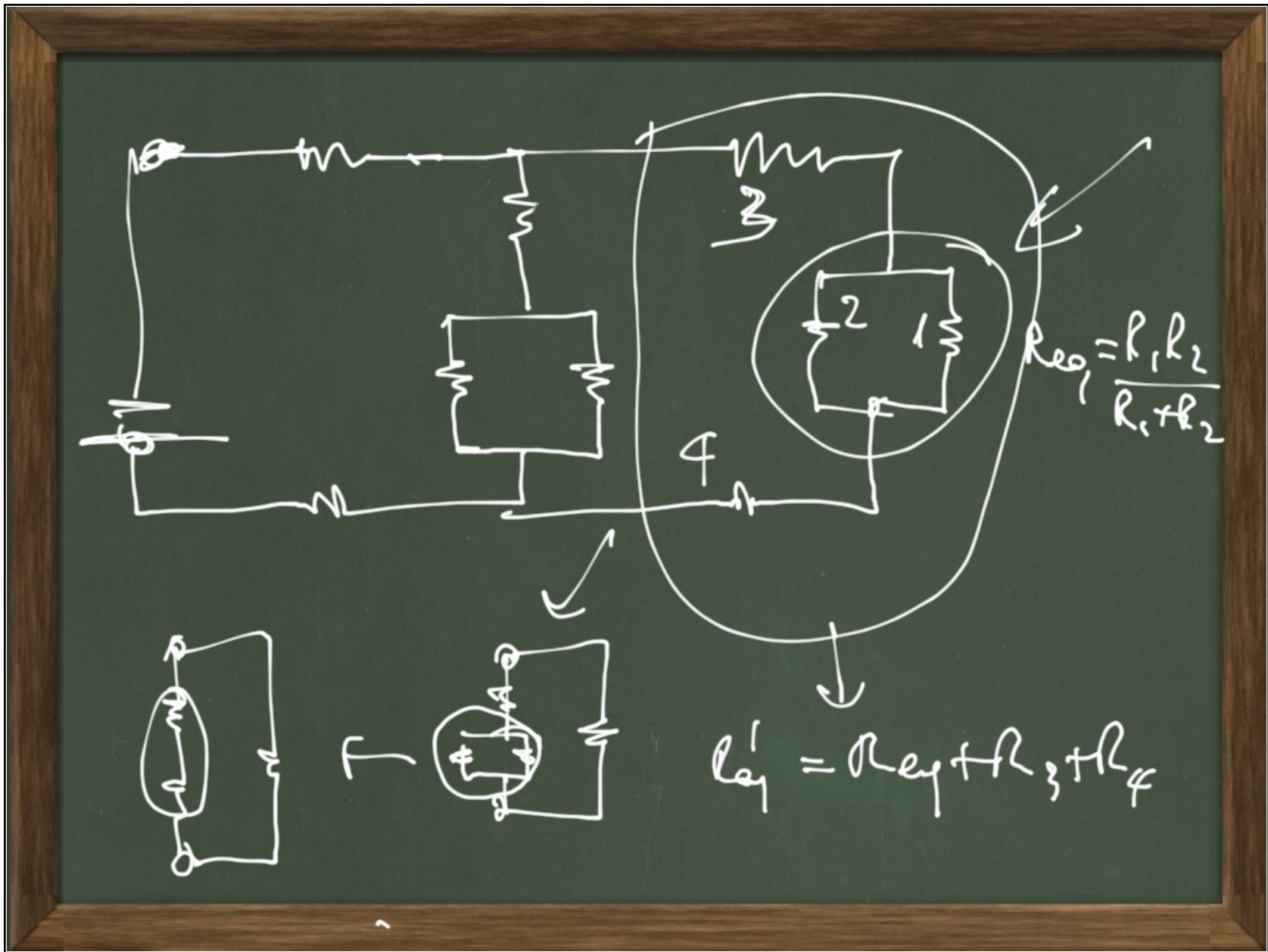

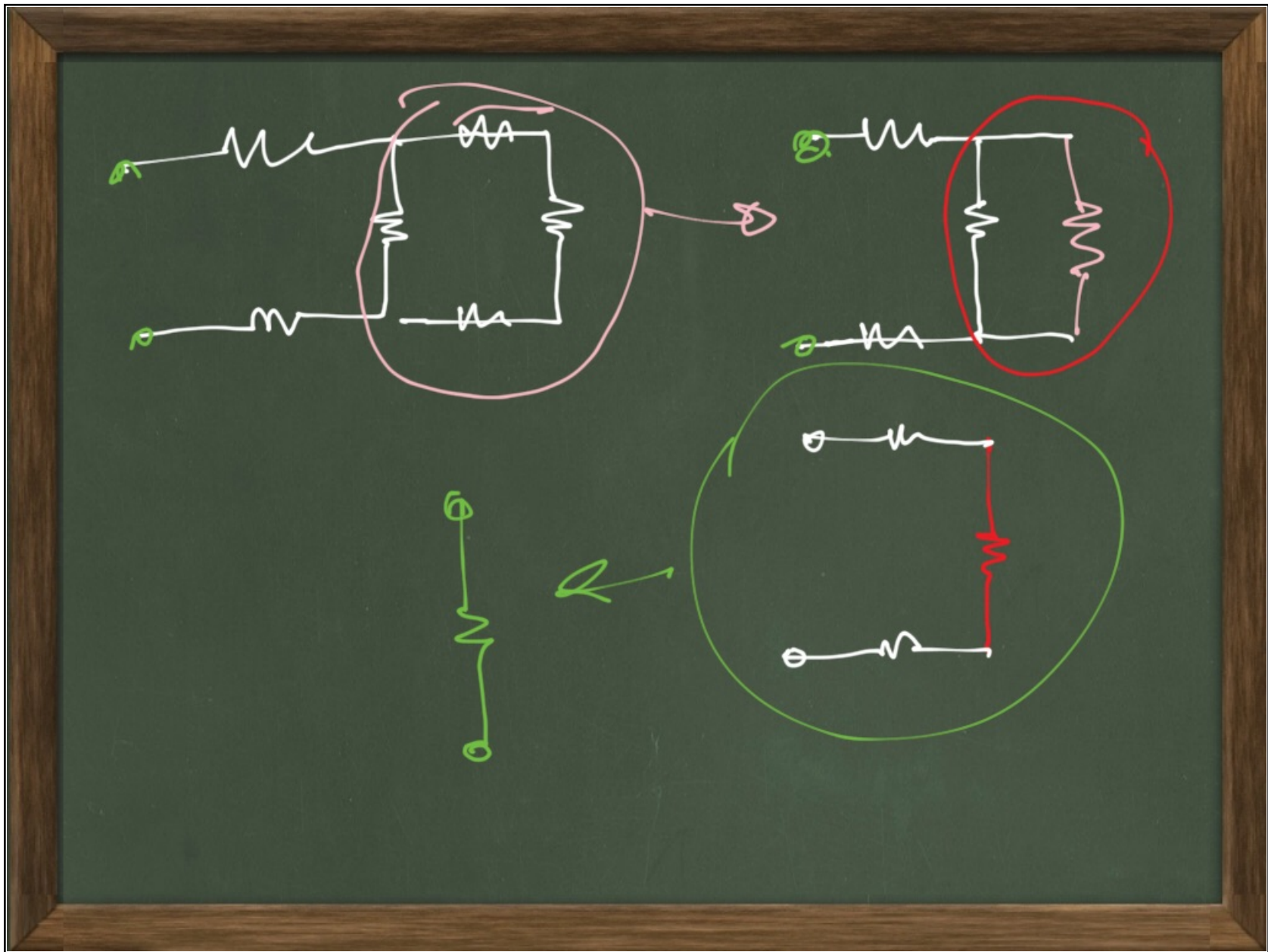

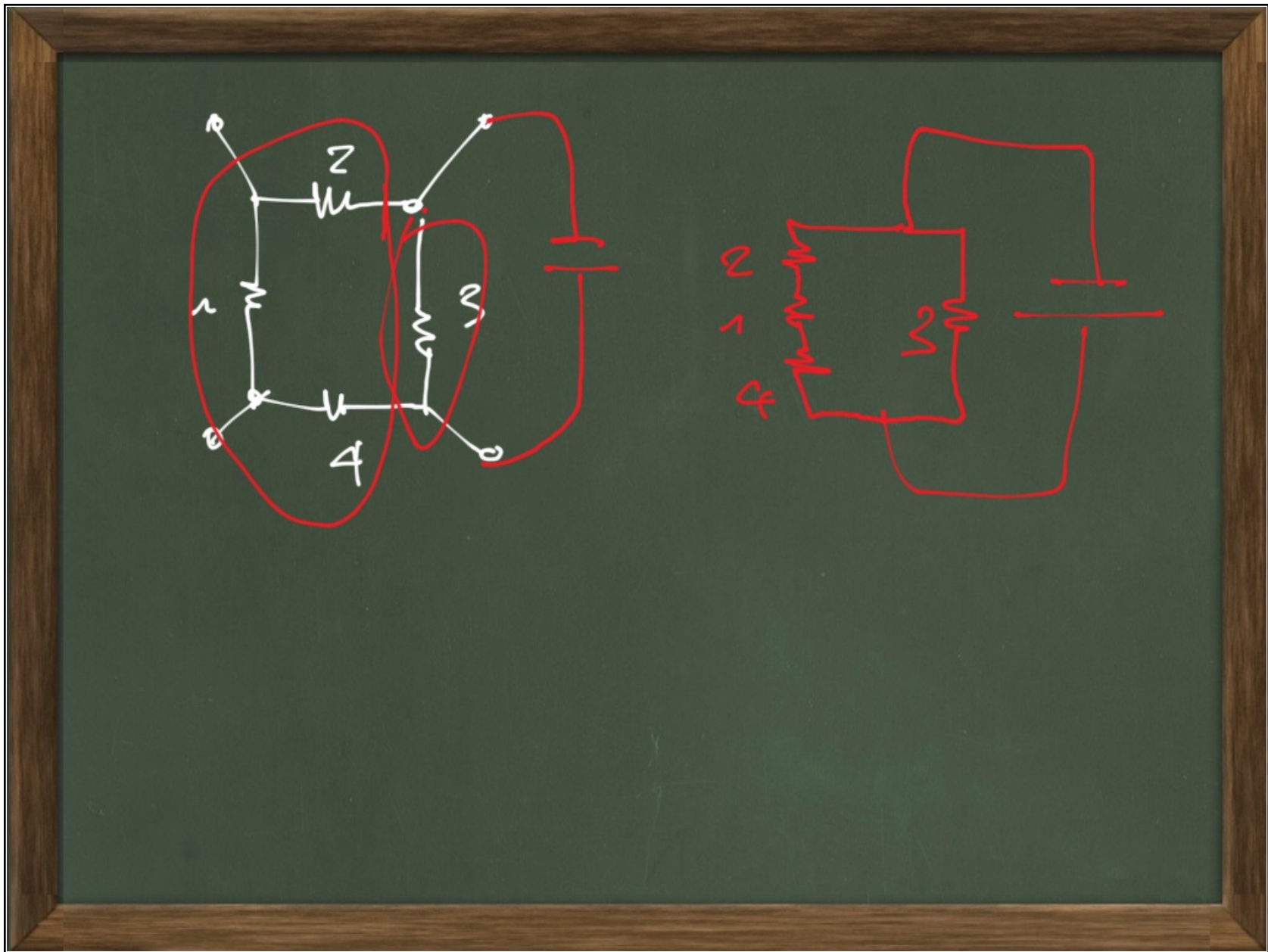

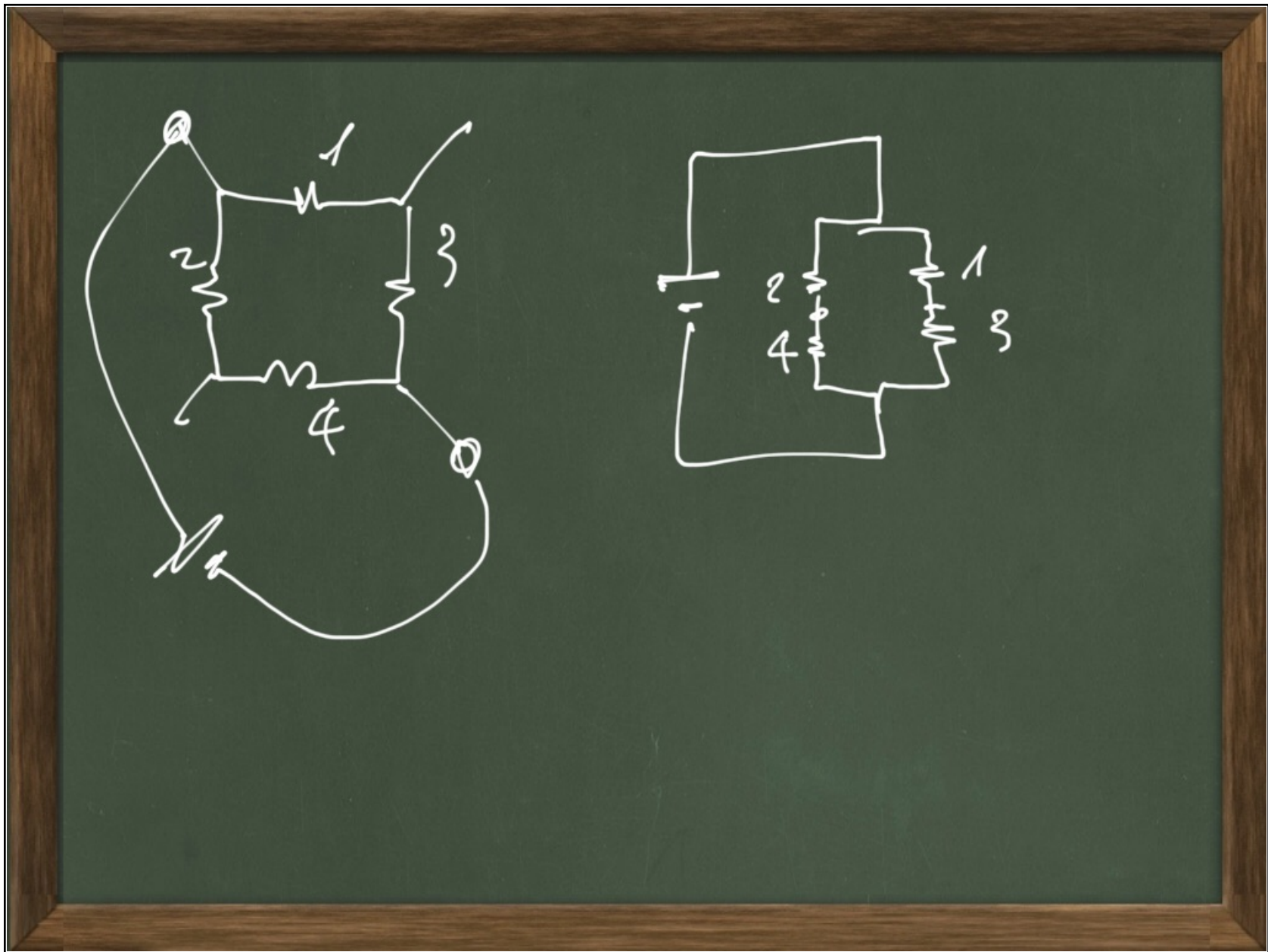

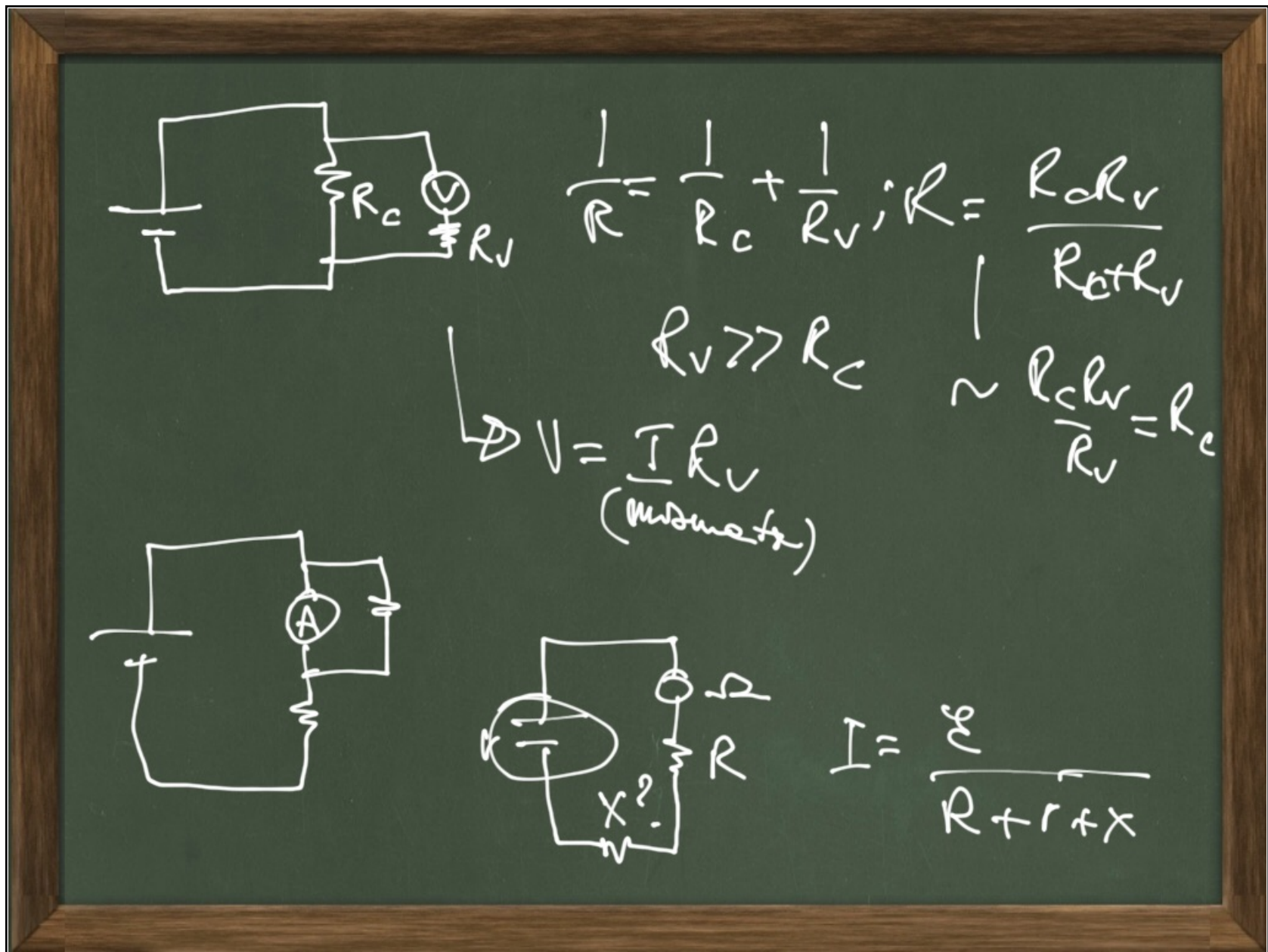

$$\frac{1}{R} = \frac{1}{R_c} + \frac{1}{R_v}; R = \frac{R_c R_v}{R_c + R_v}$$

$$R_v \gg R_c \Rightarrow R \approx R_c$$

$$V = I R_v \text{ (measured)}$$

$$I = \frac{\mathcal{E}}{R + r + X}$$

Wegfinder
 $A \rightarrow I_1$
 $\rightarrow \Delta V_{AB} = 0$

$$R_x I_x = R_1 I_1$$

$$R_3 I_x = R_2 I_1$$

$$R_x = \frac{R_3 R_1}{R_2}$$

