


RIASSUMEN DO!




RLC
non
alimentato

$$\omega_{LC} > \frac{1}{2\tau_{LR}} \sim \frac{\omega_{CR}}{2}$$
$$\tau_{RL} > \frac{\tau_{RC}}{4}$$

RLC in serie, alimentato

$$E = E_m \sin \omega t$$

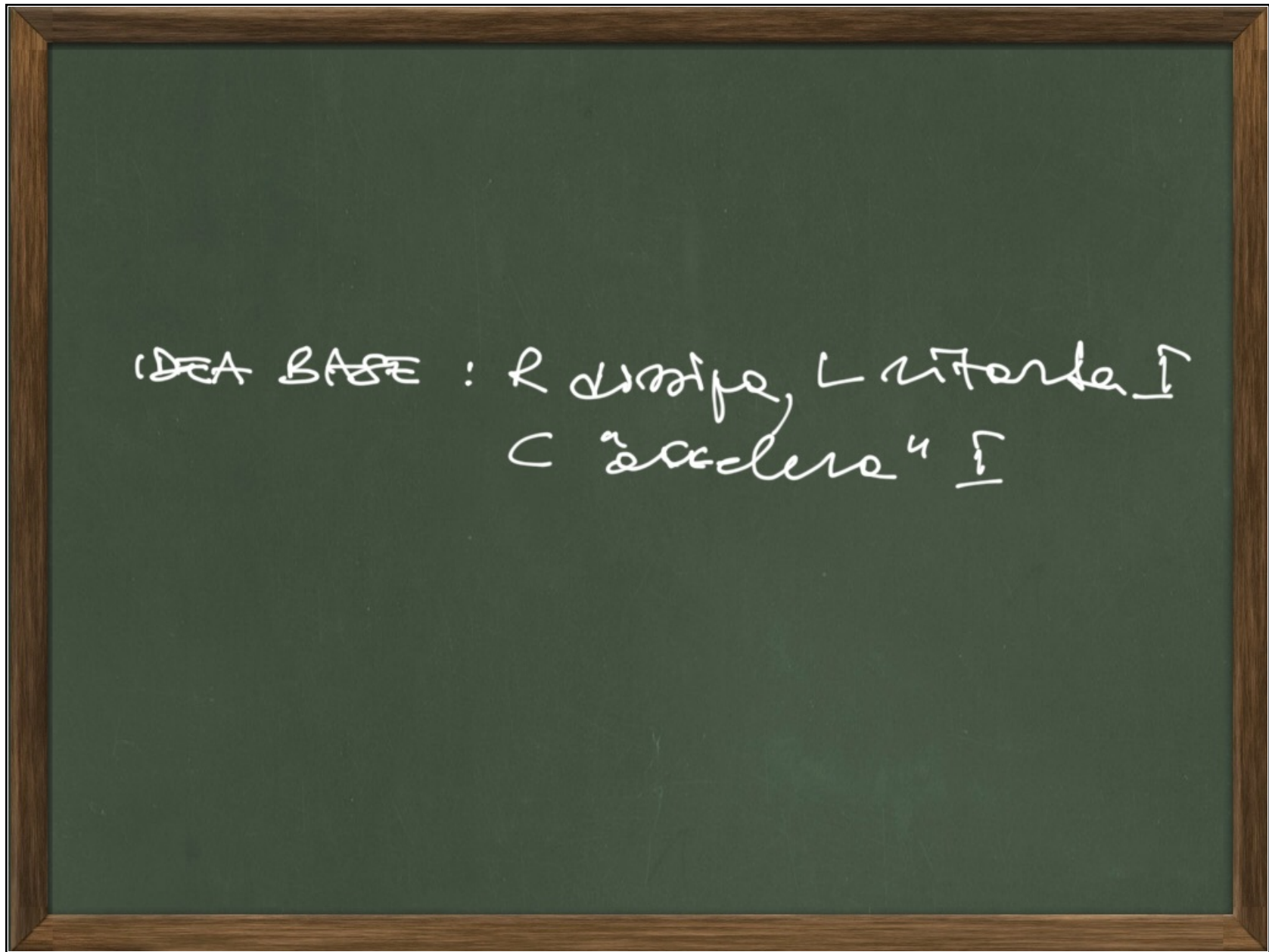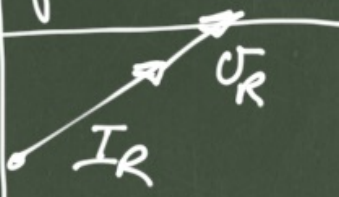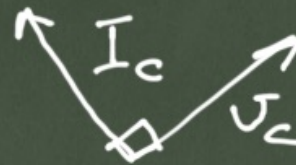

caso	I_0	"R"	fase	fasori
R	$\frac{V_R}{R}$	R	\emptyset	
C	$\frac{V_R}{X_C}$	$X_C = \frac{1}{\omega C}$	$-\frac{\pi}{2}$	
L	$\frac{V_L}{X_L}$	$X_L = \omega L$	$\frac{\pi}{2}$	

"Ohm" su C e L \Rightarrow reattanze