


$$U = U_E + U_B = \frac{q^2}{2C} + \frac{L I^2}{2}$$

$$\mathcal{H} = \frac{mv^2}{2} + \frac{kx^2}{2} \quad \frac{d\mathcal{H}}{dt} = 0 = mv \frac{dv}{dt} + kx \frac{dx}{dt}$$

$$m \cancel{v} \frac{d^2 x}{dt^2} + kx \cancel{\frac{dx}{dt}} = 0$$

$$m \ddot{x} = -kx \quad \ddot{x} = -\omega^2 x$$



$$x = x_0 \cos(\omega t + \phi) \quad \omega = \sqrt{\frac{k}{m}}$$

$$\langle U_c \rangle = \langle U_p \rangle \quad \text{VIRIALE}$$

$$U_B + U_E = \frac{L I^2}{2} + \frac{q^2}{2C}$$

$$L I \frac{dI}{dt} + \frac{q}{C} \frac{dq}{dt} = L \cancel{I} \frac{d^2 q}{dt^2} + \frac{q}{C} \cancel{I}$$

$$\ddot{q} = -\frac{1}{LC} q$$

$$\ddot{x} = -\omega^2 x$$

$$\omega_{LC} = \sqrt{\frac{1}{LC}}$$

$$q = Q \cos(\omega_{LC} t + \phi)$$

$$\phi = 0 \rightarrow t \rightarrow 0$$

$$I = -\omega_{LC} Q \sin(\omega_{LC} t + \phi)$$

cond. carica

osc	x	v	m	k	$T = \frac{2\pi}{\omega}$
LC	q	I	L	1/C	$= 2\pi\sqrt{LC}$

osc	$\omega = \sqrt{k/m}$	$m v^2 / 2$	$k x^2 / 2$
LC	$\omega = \sqrt{1/LC}$	$L I^2 / 2$	$q^2 / 2C$

Made with Doceri

$$\begin{aligned}
 V_F &= \frac{q^2}{2C} = \frac{Q^2}{2C} \cos^2 \omega t \\
 V_B &= \frac{L I^2}{2} = \frac{L \omega_{LC}^2 Q^2 \sin^2 \omega t}{2} \\
 &\frac{Q^2}{2C} \cos^2 \omega t + \frac{L \omega_{LC}^2 Q^2}{2} \sin^2 \omega t \\
 &= \frac{Q^2}{2C} (\cos^2 \omega t + \sin^2 \omega t) \leftarrow \frac{1}{LC} \frac{Q^2}{2} \\
 &= \boxed{\frac{Q^2}{2C}} = \frac{L I_0^2}{2} = \frac{L (\omega_{LC} Q)^2}{2}
 \end{aligned}$$

$$V_E = \frac{Q^2}{2\epsilon} \cos^2 \omega t \rightarrow \langle V_E \rangle = \frac{Q^2}{2\epsilon} \frac{1}{2}$$

$$V_B = \frac{L I_0^2}{2} \cos^2 \omega t \rightarrow \langle V_B \rangle = \frac{L I_0^2}{2} \frac{1}{2}$$

$$\frac{L \omega^2 Q^2}{2} = \frac{L}{2LC} Q^2 = \frac{Q^2}{2\epsilon} = \langle V_E \rangle$$

$$\frac{\epsilon \langle E^2 \rangle}{2} = \frac{\mu_0 \langle B^2 \rangle}{2} \Rightarrow \langle E^2 \rangle = \frac{\mu_0 \langle B^2 \rangle}{\epsilon_0 \mu_0}$$

$E^2 = B^2 c^2$

